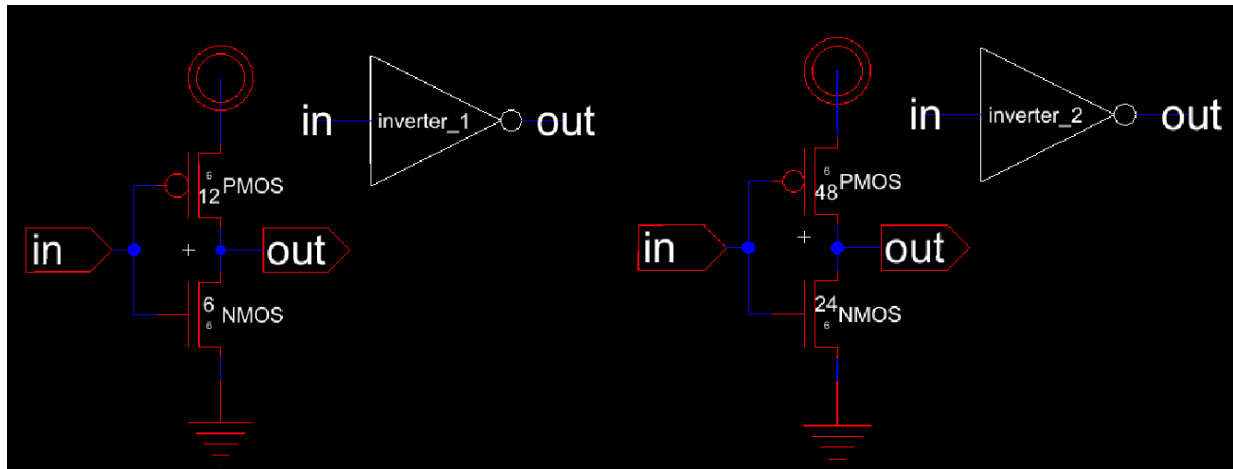


VLSI Lab 4 – Inverters



Matthew Murray – 873525242

Schematic



Inverter 1/2



Inverter Sim

 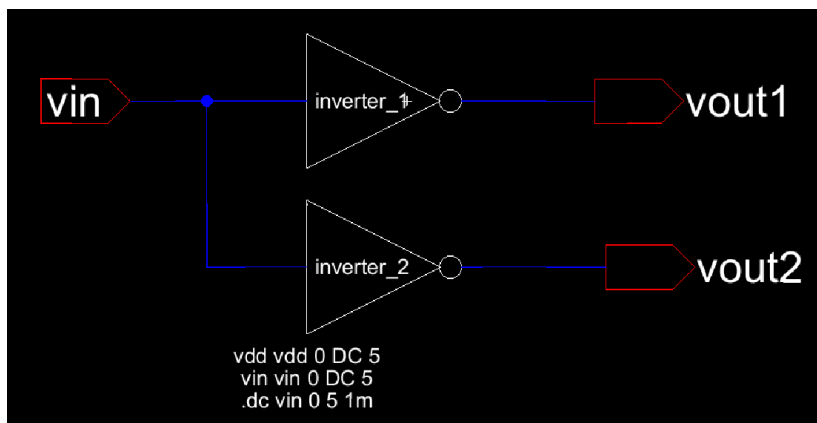


Pulse Sim

 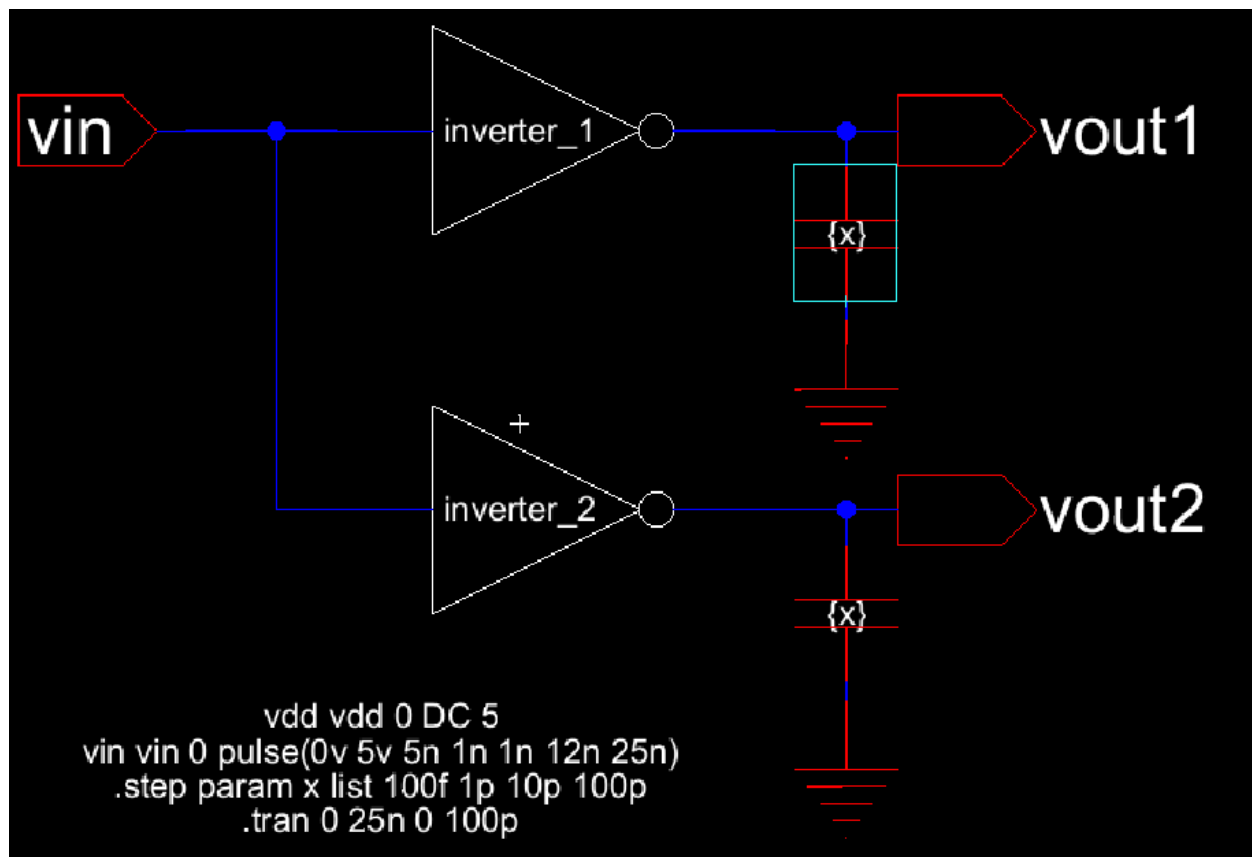

Inverter 2 appears to switch faster in both directions compared to inverter 1. Lower capacitances also appear to cause a little bit of “overshoot” during the transition where voltage goes slightly above 5V or below 0V.

Layout

Inverter ½

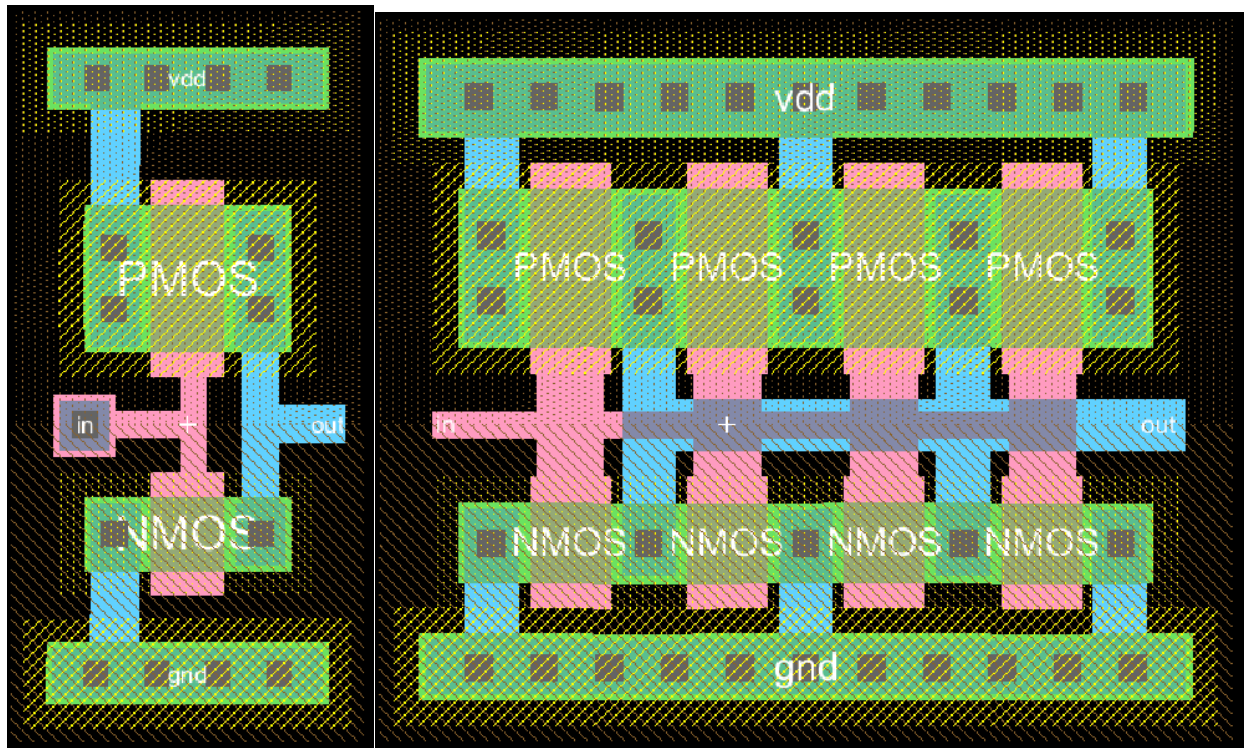

Metals and polysilicon wires were made as thick as DRC rules allow, but especially for inverter 1 it wont let it go any thicker than 2 for some reason.