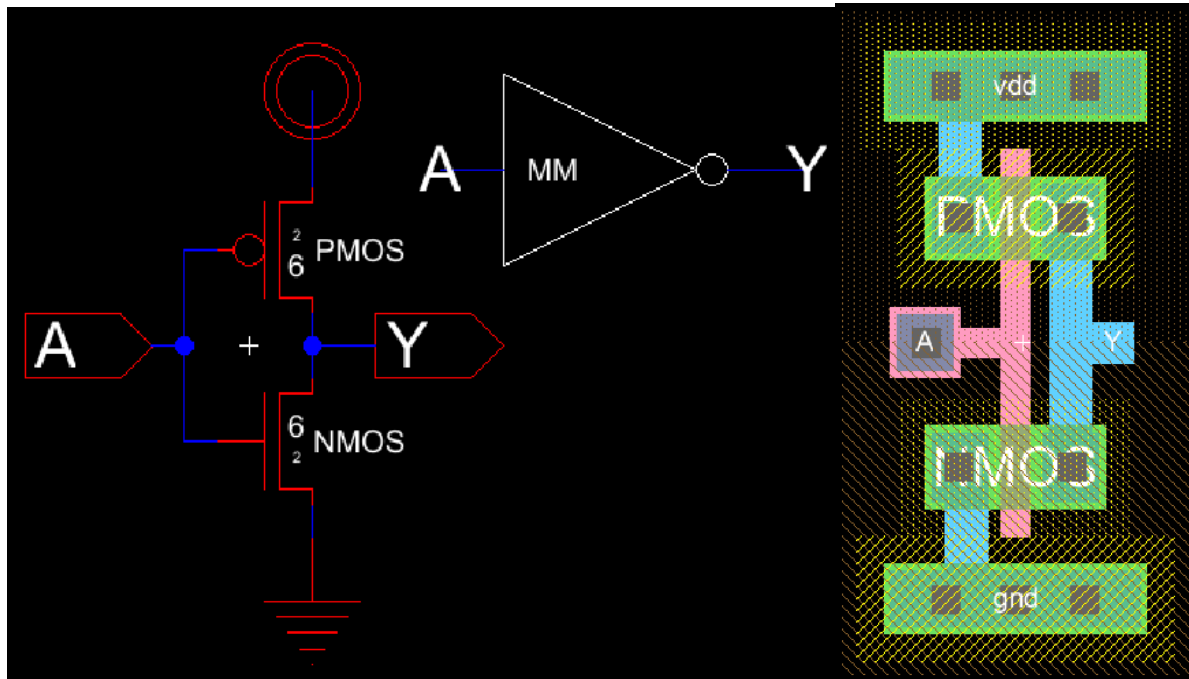



## VLSI Lab 5 – Full Adder

Matthew Murray – 873525242

Not




Logic Sim

 


Not\_out is high when va is low, and low when va is high.

## NAND


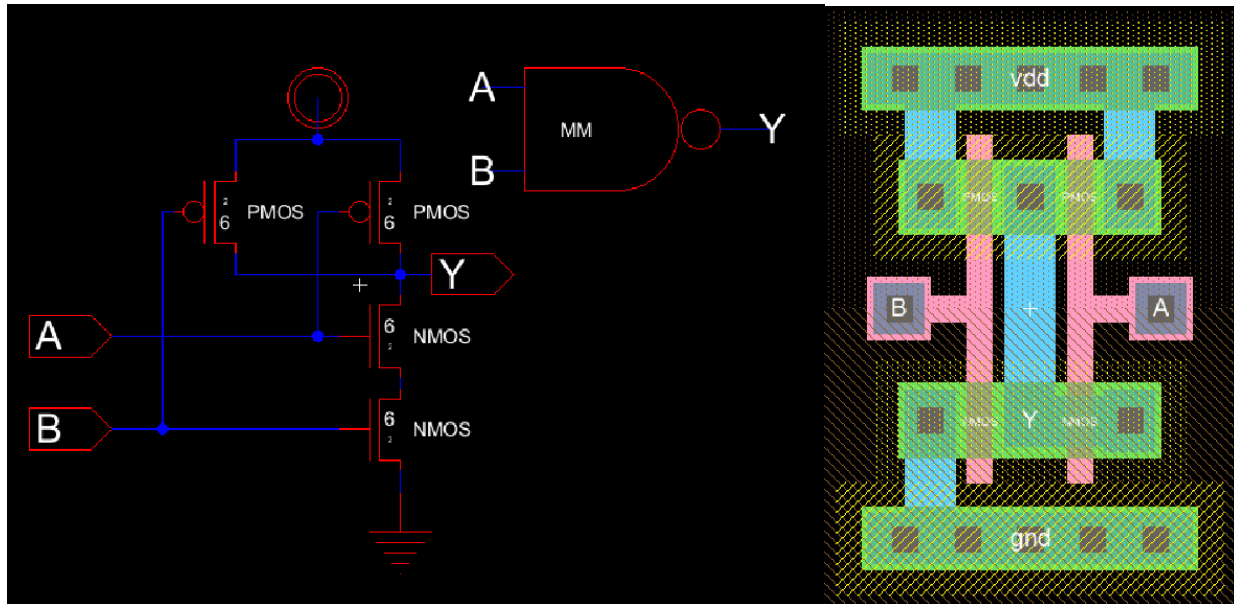


## Logic Sim

 


Nand\_out is low when both va and vb are high, and high otherwise.

# XOR

 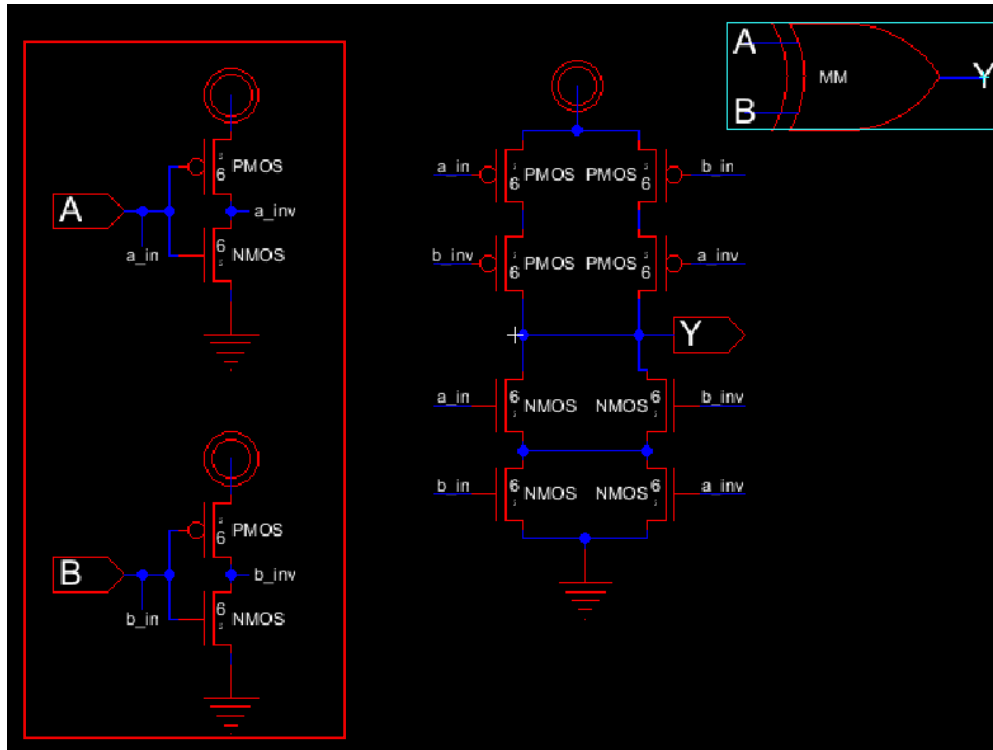


Some nets were routed on metal 2 to keep the design as compact as possible. This way all the bulk connections will line up with the inverter and NAND bulk connections for the full adder.

## Logic Sim

 



Xor\_out is high when either va or vb are high, but not with both or neither or high.

## Output Glitches

 


When both inputs change at the same time, the output can glitch in the transition zone like in the above simulation

## Full Adder

 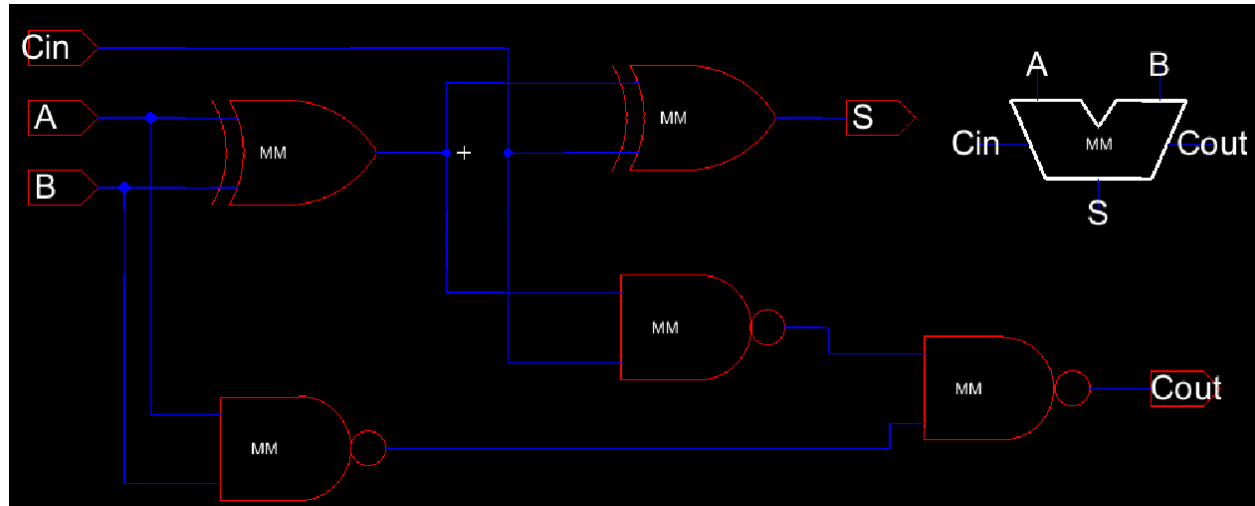

The input and outputs are the bottom 3 metal 1 lines. If these could be placed on metal 3 they could be placed on top of the adder to make a fully tileable design.

## Logic Sim

 

S is high when either 1 or 3 of the inputs (a, b, cin) are high, otherwise its low. Cout is high when 2 or 3 of the inputs are high, otherwise its low.

## DRC & NCC

```
=====6=====
Running DRC with area bit on, extension bit on, Mosis bit
Checking again hierarchy .... (0.001 secs)
Found 11 networks
0 errors and 0 warnings found (took 0.026 secs)
=====7=====
Hierarchical NCC every cell in the design: cell 'full_adder{sch}' cell 'full_adder{lay}'
Comparing: lab5_full_adder:NAND{sch} with: lab5_full_adder:NAND{lay}
  exports match, topologies match, sizes match in 0.058 seconds.
Comparing: lab5_full_adder:XOR{sch} with: lab5_full_adder:XOR{lay}
  exports match, topologies match, sizes match in 0.004 seconds.
Comparing: lab5_full_adder:full_adder{sch} with: lab5_full_adder:full_adder{lay}
  exports match, topologies match, sizes match in 0.013 seconds.
Summary for all cells: exports match, topologies match, sizes match
NCC command completed in: 0.089 seconds.
```